



# ECE 383 - Embedded Computer Systems II Lecture 10 - Datapath and Control

Lab 1: Lessons learned

- testbenches
- HW → Labs

# Lesson Outline

- Generics
  - Datapath and Control
  - Design Process
    - If
    - For
    - While
    - Assignment
  - Basic Building Blocks –  $BBBs$
- "Mini-C"*
- 
- VHDL

# Generics

## ■ Entity **Declaration:**

```
entity lec10 is
    generic(N: integer := 4);
    port(    clk: in STD_LOGIC;
              reset : in STD_LOGIC;
              ctrl: in std_logic_vector(1 downto 0);
              D: in unsigned (N-1 downto 0);
              Q: out unsigned (N-1 downto 0));
end lec10;
```

what device is this?



## ■ Note:

- The variable N is available in the entity and architecture context. In this case, you will need it to define the width of vectors.
- The value of N must be an integer, not a binary string. Just use positive integers for N.

## ■ Note:

- The default value for N is 4. That means, if you do not use the generic map statement in the instantiation below, you will get a 4-bit counter.
- The D and Q vectors use N-1 because the vector starts at 0.

## ■ Instantiation:


uut: lec10

```
generic map(5)
port map ( clk => clk,
            reset => reset,
            ctrl => ctrl,
            D => D,
            Q => Q);
```

→ see code
 
# Generics – 5-Bit Counter

- In this case, I made a 5-bit counter. The testbench linked on Lesson 10 runs the counter through all four control modes and even shows how it rolls over (around 7.5uS).



Control	Description
00	Hold
01	Count up
10	Load D
11	Synchronous Reset

Button

Action



World Record for presses per second? \_\_\_\_\_

\_\_\_\_\_ msec

Can use this generic counter twice in HW07

①  $N=4$

$$\text{Clock} = 100 \text{ MHz}$$

$$\text{so } T = \frac{1}{100 \text{ MHz}} = \underline{\quad}$$

②  $N = ?$

How many counts for 20 msec?

\_\_\_\_\_

Simulation Time issue?

TB has 100 kHz option

See hw07\_tb

# Datapath and Control

BBBs

STATEMACHINE

sw = status word

cw = control word

# Datapath and Control

- Datapath and Control Design Methodology
  - Datapath - responsible for data manipulations
  - Control - responsible for sequencing the actions of the datapath

BBBs

FSM

 


Fig 10.0 - An abstract digital system constructed from a datapath and a control unit.

# Design Process

# Design Process

Step 0:

- Building digital systems using the datapath and control approach is a three-step process.

1. Write an algorithmic description for the solution to the problem. "Mini-C"
2. Parse the algorithmic description into datapath building blocks and control states.
3. ~~Define the MIEs and OEs for the control unit.~~ **Nope!**

- (a) State Transition Diagram
- (b) State Output Table      cw    sw  
                                ↓        ↑
- (c) Datapath (BBBs)

- The programming language used to formalize an algorithmic solution to design problem is referred to as mini-C (a derivative of the C-programming language)
  - **IF**  
if (condition) then BODY\_1 else BODY\_2
  - **FOR**  
for (i=A; i<B; i += 1) BODY
  - **WHILE**  
while(condition) BODY
  - **ASSIGNMENT**  
 $X = \text{value};$        $X = (A + B) >> 4;$

# Design Process – If/Then/Else

```

if (x == y) {
  Body1;
} else {
  Body2;
}
  
```

How to make comparator?  
 Process or CSA?

 


Fig 10.1 - The datapath and control components required to realize an if/then/else structure.

# Design Process – For Loop

for ( $i=7; i<14; i++$ ) {

  Body;

  }

Counter control?

{  
  cw  
  00  
  01  
  10  
  11

How to implement counter?

How to implement comparator?

 


Fig 10.2 - The datapath and control components required to realize a for loop.

# Design Process – While Loop

while ( $x == y$ ) {  
 Body;  
}

How to implement comparator?

 


Fig 10.3 - The datapath and control components required to realize a while statement.

# Design Process - Assignment

or Operation

$$X = X + Y;$$

How to implement?

Adder?

X Register?

 



Fig 10.5 - The datapath and control components required to realize an assignment statement of the form  $X=X+Y$ .

# Basic Building Blocks

# Basic Building Blocks

Device	Data in	Data out	Status	Control
N:M Decoder	1 bit	M bits		N bits
N:1 Mux	N bits	1 bit		$\log_2(N)$ bits
M-bit N:1 Mux	N, each M-bits	M bits		$\log_2(N)$ bits
N-bit adder	2, each N-bits	N bits	Overflow	
N-bit add/sub	2, each N-bits	N bits	Overflow	1 bit
N-bit comparator	2, each N-bits		3 bits	
BCD to 7-segment	4 bits	7 bits		
N-bit priority encoder	N bits	$\log(N)$ -bits		
N-bit register	N bits	N-bits		1 bit
N-bit shift register	N bits	N-bits		2 bits
N-bit counter	N bits	N bits		2 bits
Three state buffer	N bits	N bits		1 bit
N:M RAM	$\log_2(N)$ bits, M bits	M bit		2 bits
N-bit Bus transceiver	N bits	N bits		2 bit

Table 10.6 - The list of all the basic building blocks and some of their attributes.

 

$$2^n = 128 \quad n = \underline{\hspace{2cm}}$$

# Handout Problem

Step 0

**Minimum Search** Design a digital circuit that looks for the smallest 8-bit integer in a 128x8 bit RAM. The numbers are stored at addresses 0...99, you may assume that the RAM is preloaded with data.


Step 1

1. min = 0xFF; // Set the min reg to largest value
2. for (i=0; i<100; i++) { // Search through the entire array
3.     MBR=RAM[i]; // read an 8-bit value from the RAM
4.     if (MBR<min) then // If MBR is smaller than min
5.         min = MBR; // then set min to the smallest value
6. } // end for


variables are

Step 2

## FSM – State machine Control

 


## BBBs – Basic Building Blocks Datapath

 

# CW output table

State	CS	RE	WE	Reg Min	Min mux	Counter	MBR
	0 off	0 idle	0 idle	0 hold	0 load FF	00 hold	0 hold
	1 active	1 read	1 write	1 load	1 load RAM	01 load	1 load
						10 count	
						11 reset	
InitMin							
InitI							
CompC							
<u>Read I</u>							
CompM							
NewMin							
Inc							
Done							

**READ2**

 

- Do we need to now go and find the state transition equations and state output equations?


```

1 -----
2 -- Name:      Chris Coulston
3 -- Date:      Jan 28, 2015
4 -- File:      lec09.vhd1
5 -- Event:     Lecture 9
6 -- Crs:       ECE 383
7 -----
8 library IEEE;
9 use IEEE.STD_LOGIC_1164.ALL;
10 use IEEE.NUMERIC_STD.ALL;
11
12 entity lec09 is
13     Port( clk: in STD_LOGIC;
14            reset : in STD_LOGIC;
15            sw: in STD_LOGIC_VECTOR(2 downto 0);
16            cw: out STD_LOGIC_VECTOR(4 downto 0));
17 end lec09;
18
19 architecture behavior of lec09 is
20
21     type state_type is (WaitEnter, WaitRead, Set30, WaitLeave, Set3, Goose);
22     signal state: state_type;
23
24     constant rfid: integer := 2;           -- helps keep status bits straight
25     constant cow: integer := 1;
26     constant timer: integer := 0;
27
28 begin
29     state_process: process(clk,reset)
30     begin
31         if (rising_edge(clk)) then
32             if (reset = '0') then
33                 state <= WaitEnter;
34             else
35                 case state is
36                     when WaitEnter =>
37                         if (sw(cow) = '1') then state <= WaitRead; end if;
38                     when WaitRead =>
39                         if (sw(rfid) = '1') then state <= Set30; end if;
40                     when Set30 =>
41                         state <= WaitLeave;
42                     when WaitLeave =>
43                         if (sw(cow) = '0') then state <= WaitEnter;
44                         elsif (sw(timer) = '1' and sw(cow) = '1') then state <= Set3; end if;
45                     when Set3 =>
46                         state <= Goose;
47                     when Goose =>
48                         if (sw(timer) = '1') then state <= Set30; end if;
49                 end case;
50             end if;
51         end if;
52     end process;
53
54     cw <=    "10000" when state = WaitEnter else
55             "00000" when state = WaitRead else
56             "01010" when state = Set30 else
57             "01110" when state = WaitLeave else
58             "01100" when state = Set3 else
59             "01111"; -- when state = Goose;
60
61 end behavior;
62
63


```



 - Lesson 9 State Machine style?
- Lesson 10 Mini-C method?



## Button Debouncer... statemachine with delays

```
action = 0;

while (button == 0);                                // wait for button press


for (i=0; i < 20_msec_count; i++);    // delay 20 msec for bouncing to stop

while (button == 1);                                // wait for button release

for (i=0; i < 20_msec_count; i++);    // delay 20 msec for bouncing to stop

action = 1;                                         // do the action for the button event

 action = 0;                                         // undo the action for the button event
```



## How to do...

```
while (button == 1); Easy Way
```

```
action = 0;
```

```
action = 1;
```

```
action = 0;
```

2 ways

(1)

(2)

★ Testbench... 100 MHz vs 100 KHz clock

# HW06 solution?

Asynch Reset

